

CSE350: Digital Electronics & Pulse Techniques

Lecture 04: Signal Generator - Square and Triangular Wave

Course Instructor:



*MD. ZAYED BIN ZAHIR ARJU (ZBH), ADJUNCT LECTURER
Department of Computer Science and Engineering (CSE)
BRAC University*

Signal Generator

We will study two types of signal generator

- i. Square wave generator
- ii. Triangular wave generator

Basic RC Circuit Overview

We know for capacitor, $I_C = C \frac{dV_C}{dt}$

From the circuit,

$$\frac{V_C - V_S}{R} + C \frac{dV_C}{dt} = 0$$

$$\Rightarrow \int_{V_C(t_1)}^{V_C(t_2)} \frac{dV_C}{V_C - V_S} = -\frac{1}{RC} \int_{t_1}^{t_2} dt$$


$$\Rightarrow V_C(t_2) = V_S + (V_C(t_1) - V_S) e^{-\left(\frac{t_2 - t_1}{\tau}\right)}$$

We can see if $t_2 \rightarrow \infty$, then, $V_C(\infty) = V_S$

If $t_1 = 0, t_2 = t, \tau = RC$

we can simply use this form,
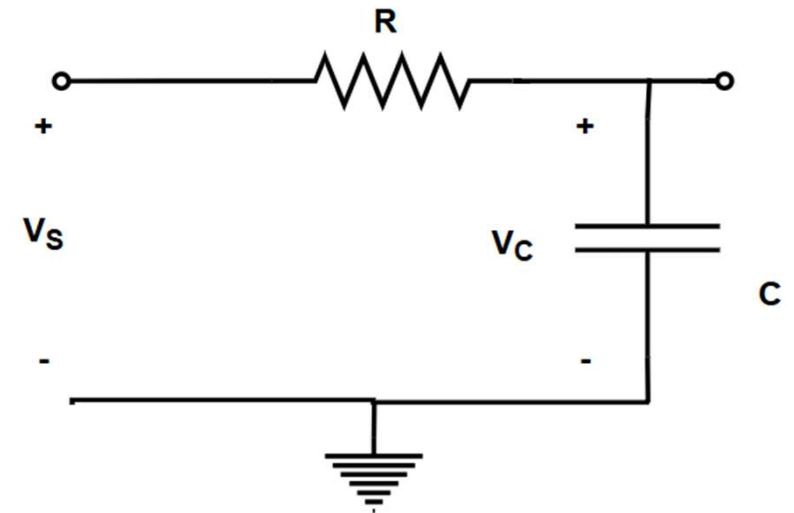
$$V_C(t) = V_C(\infty) + (V_C(0) - V(\infty)) e^{-\frac{t}{\tau}}$$



Square Wave Generator

$$\Rightarrow V_C(t_2) = V_s + (V_C(t_1) - V_s) e^{-\left(\frac{t_2-t_1}{\tau}\right)}$$

Here is the square wave generator, for it -

$$\Rightarrow V_x(t_2) = V_o + (V_x(t_1) - V_o) e^{-\left(\frac{t_2-t_1}{\tau}\right)}$$

$$\Rightarrow V_x(t_2) - V_o = (V_x(t_1) - V_o) e^{-\left(\frac{t_2-t_1}{\tau}\right)}$$

$$\Rightarrow \frac{V_x(t_1) - V_o}{V_x(t_2) - V_o} = e^{\left(\frac{t_2-t_1}{\tau}\right)}$$

$$\Rightarrow t_2 - t_1 = \tau \ln \frac{V_o - V_x(t_1)}{V_o - V_x(t_2)} \text{ -----(i)}$$


We already know from
Inv. Schmitt Trigger

Higher threshold voltage,

$$V_{TH} = V_H \frac{R_1}{R_1 + R_2}$$

Lower threshold voltage,

$$V_{TL} = V_L \frac{R_1}{R_1 + R_2}$$

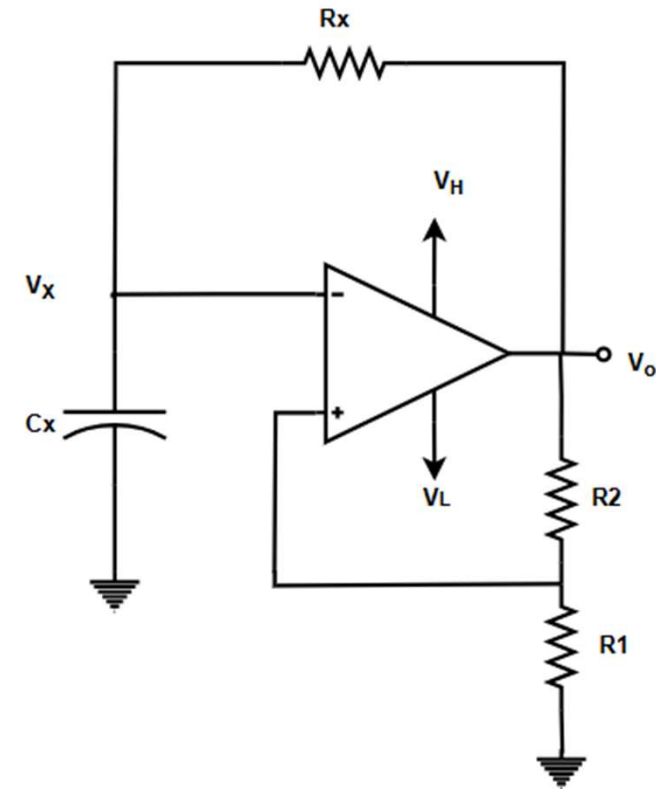

Square Wave Generator


Case 01: $0 < t < T_1$

Initially,

$$V_x(t = 0) = V_{TL} \text{ and, } V_o = V_H$$

*Untill, $V_x < V_{TH}$,
the output will remain at V_H*

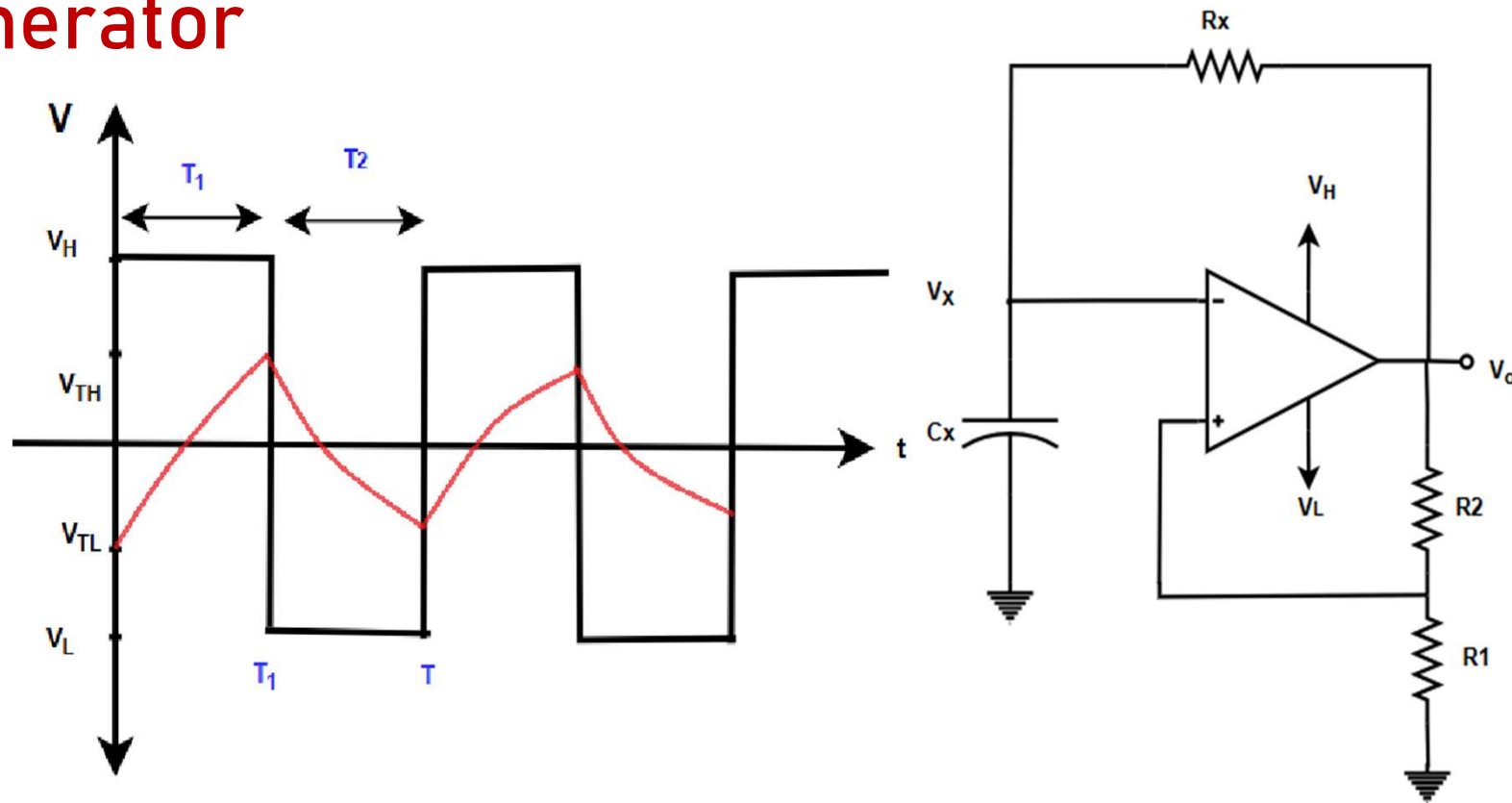But when $V_x > V_{TH}$ output
will change.





Square Wave Generator

We can use eq (i),

$$t_2 = T_1, \text{ and } t_1 = 0$$

$$T_1 - 0 = \tau \ln \frac{V_o - V(0)}{V_o - V(T_1)}$$
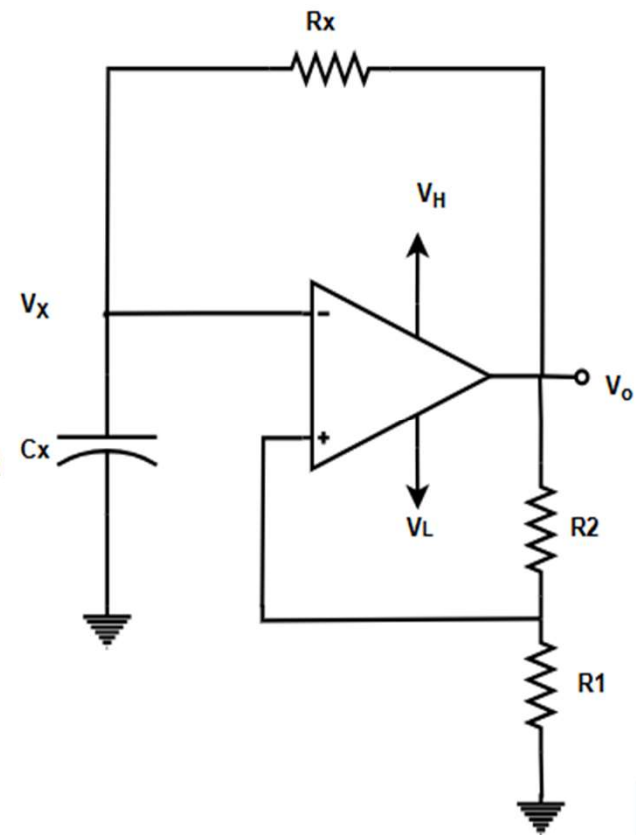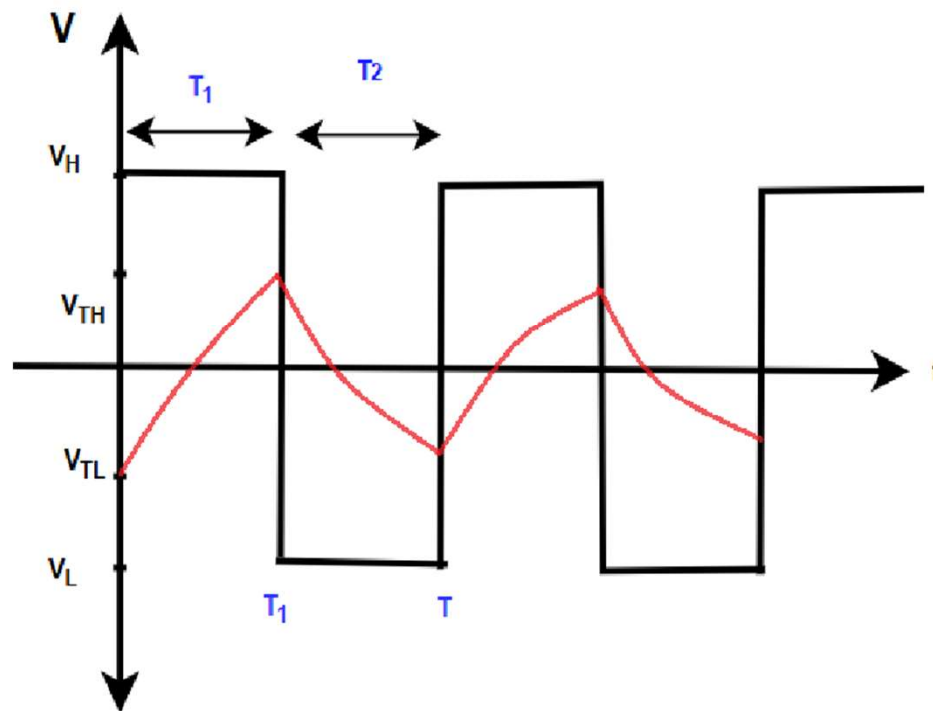
$$T_1 = R_x C_x \ln \frac{V_H - V_{TL}}{V_H - V_{TH}}$$



Square Wave Generator

Case 02: $T_1 < t < T$


Initially,

$$V_x(t = T_1) = V_{TH}$$

and, $V_o = V_L$

*Untill, $V_x > V_{TL}$,
the output will remain at V_L*

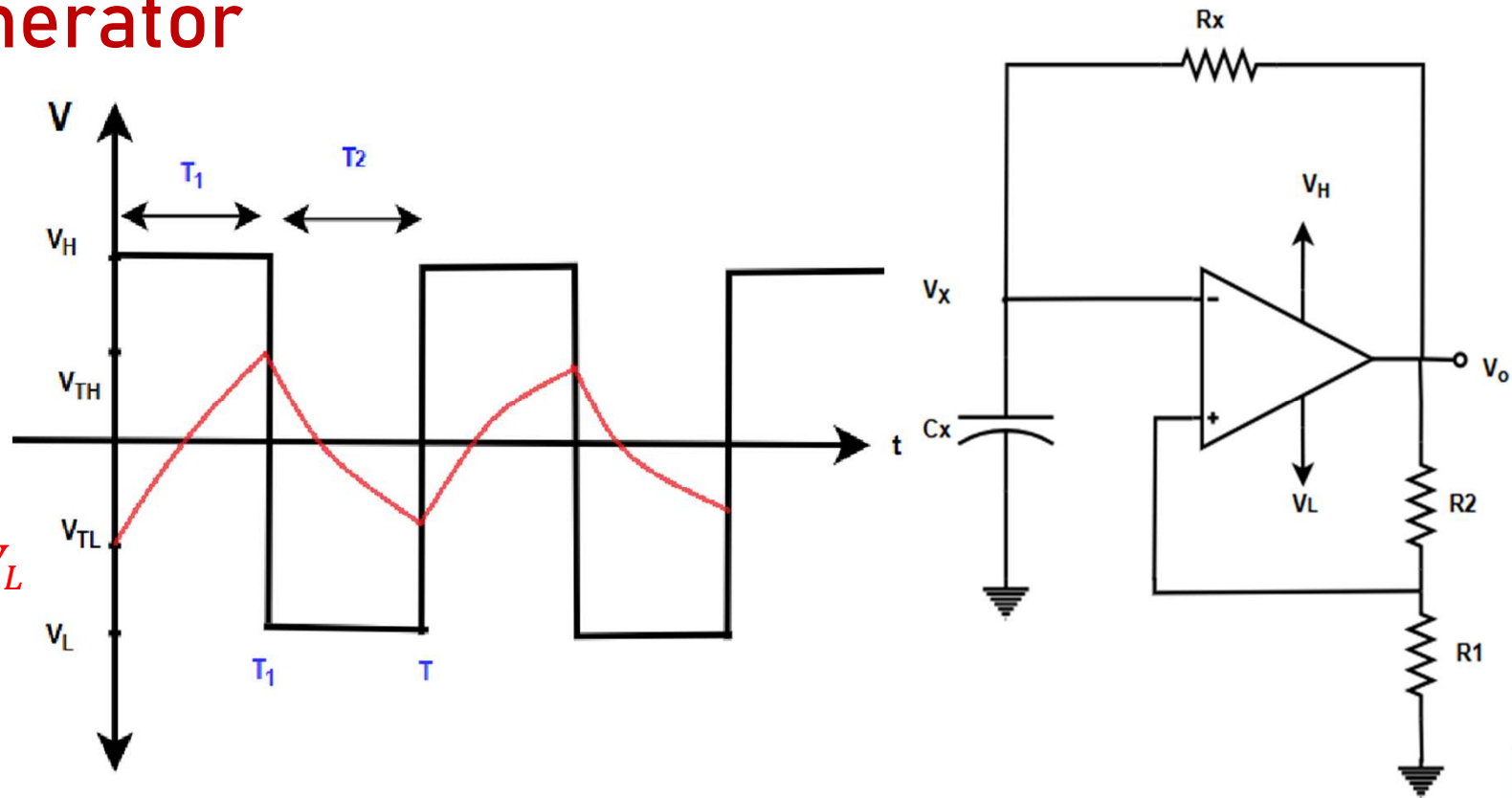But when $V_x < V_{TL}$ output
will change.





Square Wave Generator

We can use eq (i),

$$t_2 = T, \text{ and } t_1 = T_1$$

$$T - T_1 = \tau \ln \frac{V_o - V(T_1)}{V_o - V(T)}$$
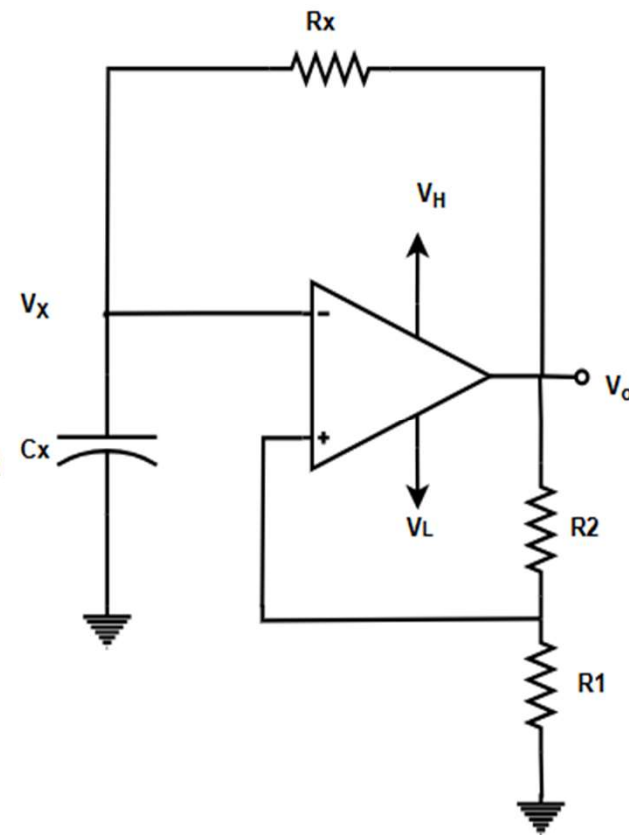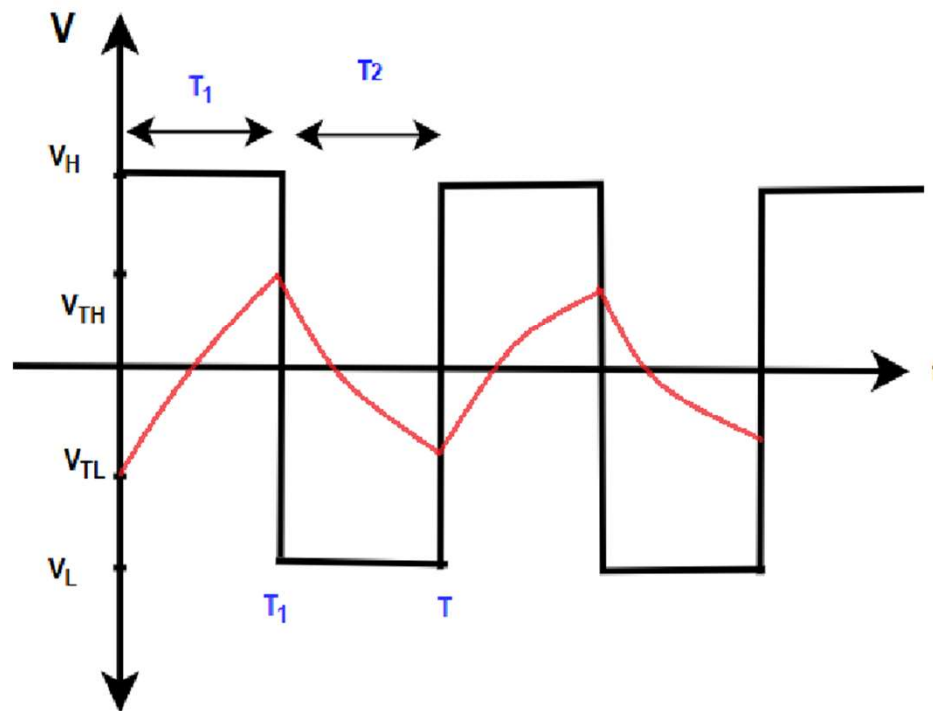
$$T_2 = R_x C_x \ln \frac{V_L - V_{TH}}{V_L - V_{TL}}$$



Square Wave Generator Formulas


$$V_{TL} = V_L \frac{R_1}{R_1 + R_2}$$

$$V_{TH} = V_H \frac{R_1}{R_1 + R_2}$$

$$T_2 = R_x C_x \ln \frac{V_L - V_{TH}}{V_L - V_{TL}}$$

$$T_1 = R_x C_x \ln \frac{V_H - V_{TL}}{V_H - V_{TH}}$$
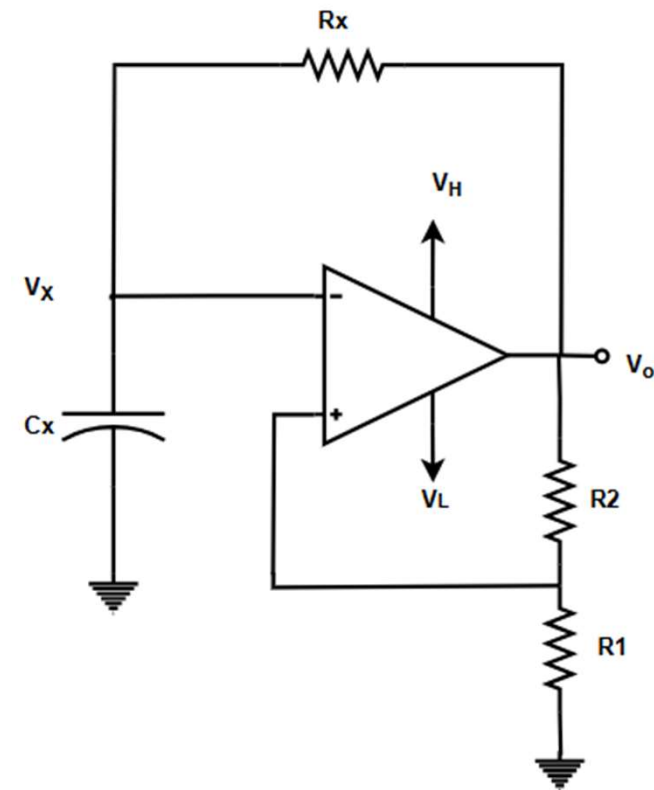
$$\text{Duty cycle} = \frac{T_1}{T_1 + T_2} * 100\% \text{ or } \frac{T_1}{T} * 100\%$$




Exercise

For the Schmitt-trigger oscillator the saturation output voltages are +10V and -5V.

$R_1 = R_2 = 20\text{ k}\Omega$ and $C_x = 0.01\text{ }\mu\text{F}$ and $R_x = 10\text{ k}\Omega$.

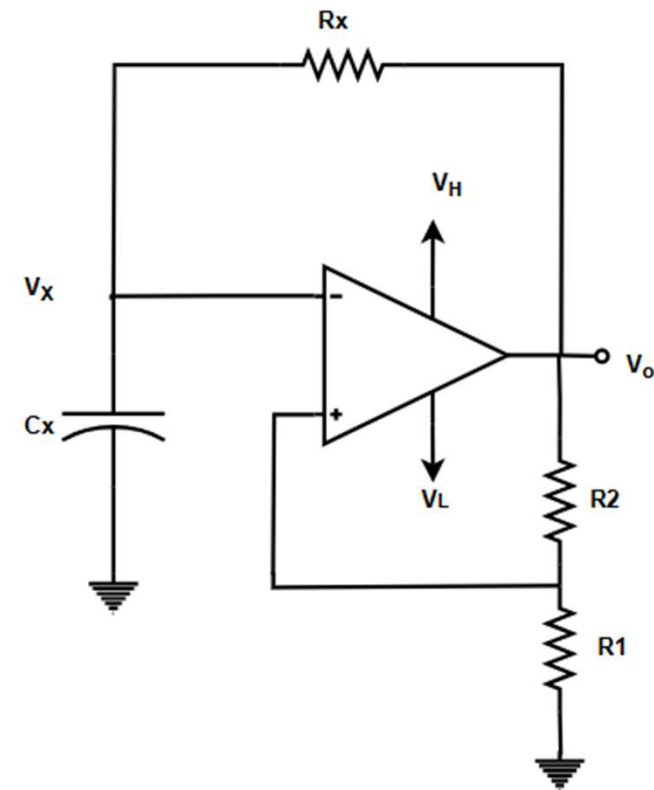
Determine the frequency of oscillation and duty cycle.



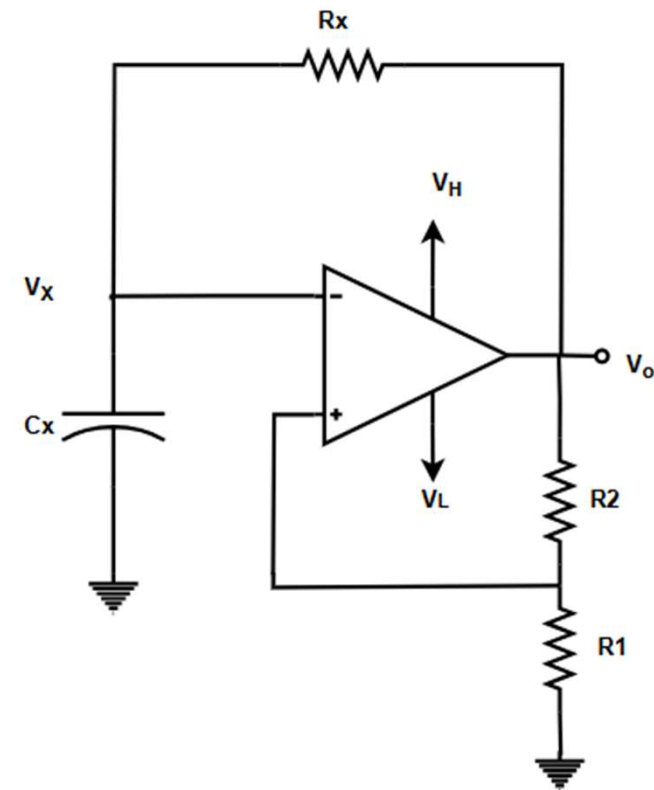Exercise


Find the **duty cycle** of the oscillator if the power supply of the OP-AMP is symmetrical.

[Hints: Symmetrical power supply $V_H = +V_{\text{sat}}$ and $V_L = -V_{\text{sat}}$]



Triangular Wave Generator

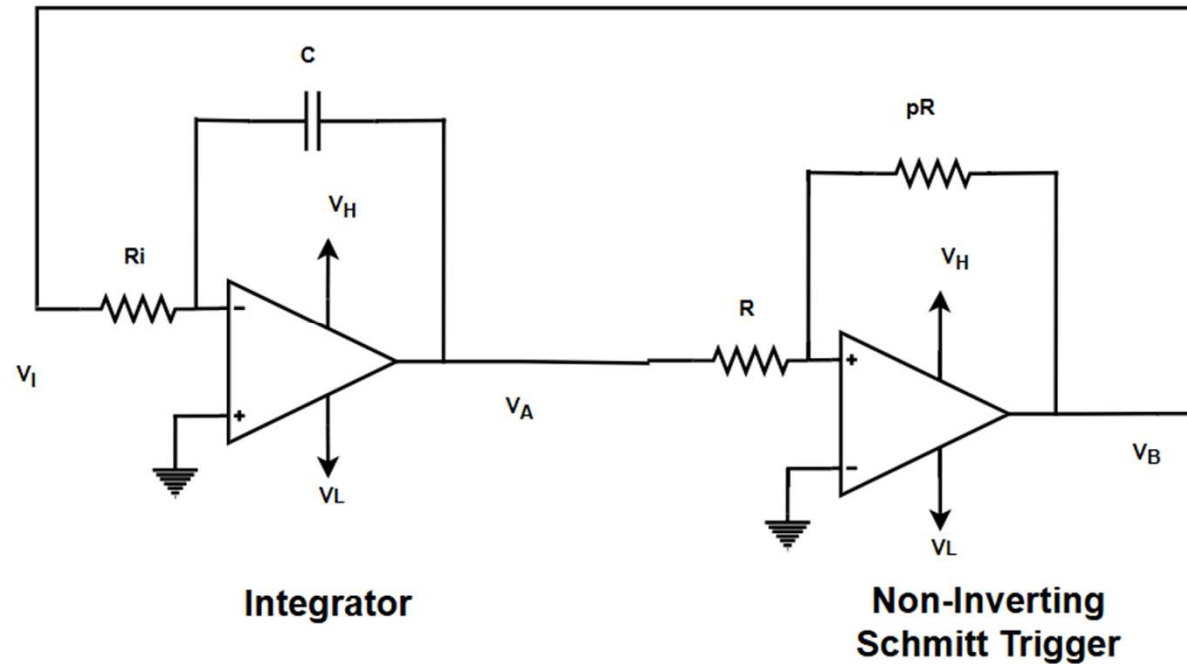Here is the circuit of the triangular wave generator.




Integrator

$$\text{Here, } I_C = C \frac{dV_C}{dt} = \frac{0 - V_S}{R_i}$$

V_S is a constant voltage.

$$\Rightarrow \int_{V_{initial}}^{V_C} \frac{dV_C}{V_S} = -\frac{1}{R_i C} \int_{t_1}^t dt$$

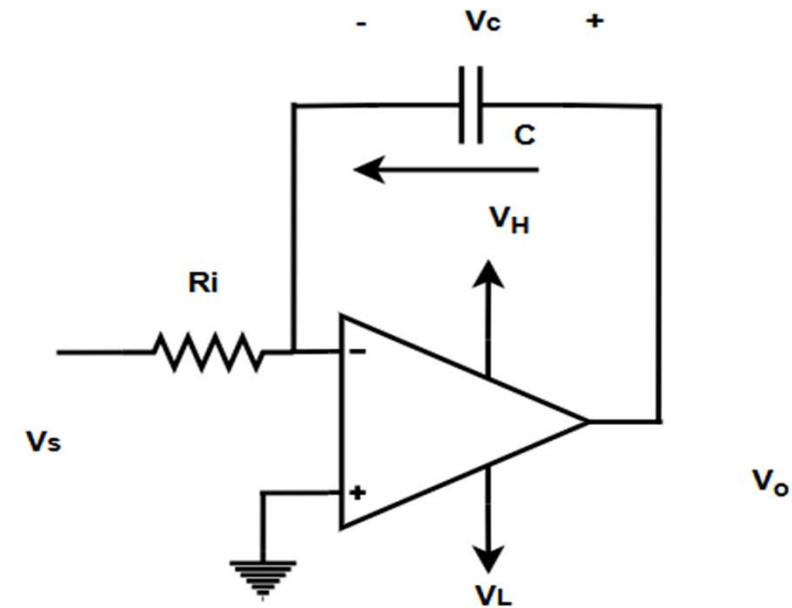
$$V_C(t) = V_{initial} - \frac{V_S}{R_i C} (t - t_i)$$



Integrator

Triangular Wave Generator

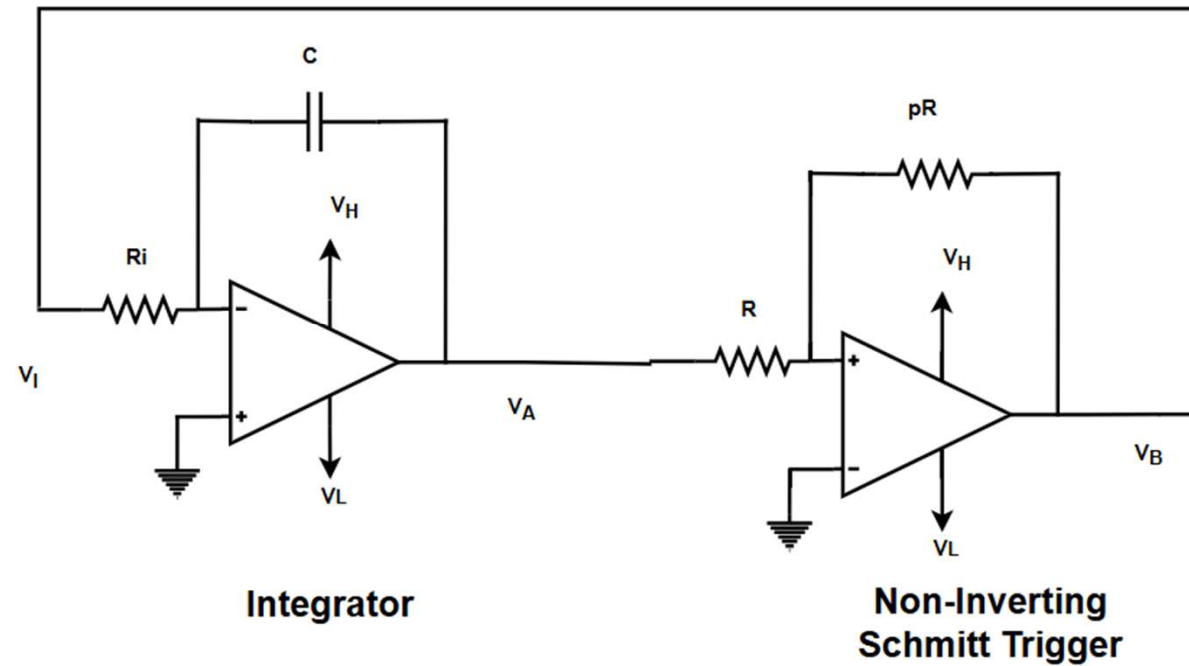Here is the circuit of the triangular wave generator.




Triangular Wave Generator

$$\begin{aligned} V_{TH} &= -\frac{R_1}{R_2} V_L \\ &= -\frac{R}{pR} V_L = -\frac{V_L}{p} \end{aligned}$$

Likewise,

$$V_{TL} = -\frac{V_H}{p}$$

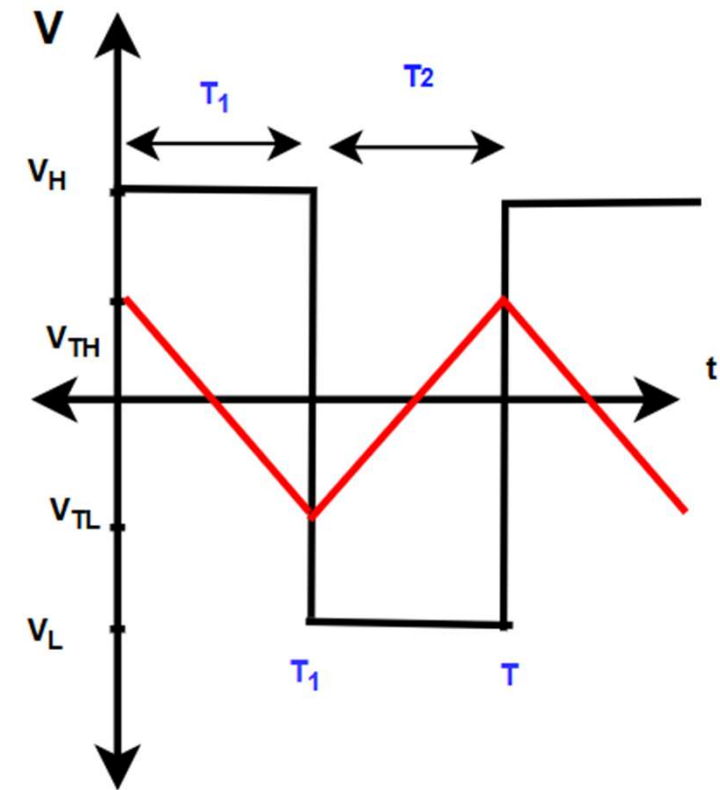

Triangular Wave Generator

Case 01: $0 < t < T_1$


$$V_C(t) = V_{initial} - \frac{V_S}{R_i C} (t - 0)$$

$$V_C(T_1) = V_{TL} \text{ and } V_C(0) = V_{TH}$$

$$T_1 = R_i C \left(\frac{V_{TH} - V_{TL}}{V_H} \right)$$

Case 02: $T_1 < t < T$
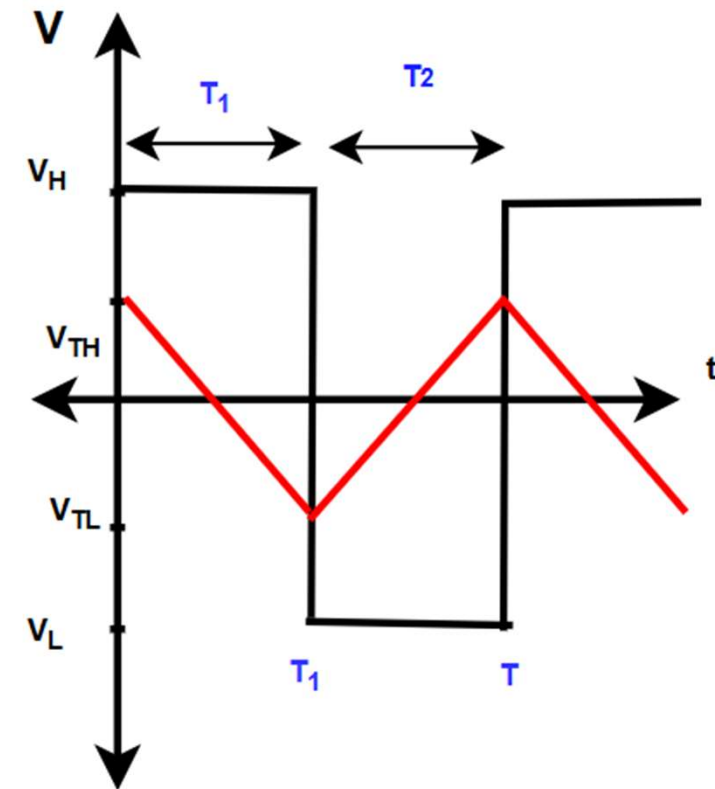
$$\text{Similarly, } T_2 = R_i C \left(\frac{V_{TL} - V_{TH}}{V_L} \right)$$



Triangular Wave Generator

$$P = \frac{R_2}{R_1}, \quad V_{TH} = -\frac{V_L}{p}$$

$$, \quad V_{TL} = -\frac{V_H}{p}$$

$$T_1 = R_i C \left(\frac{V_{TH} - V_{TL}}{V_H} \right)$$

$$T_2 = R_i C \left(\frac{V_{TL} - V_{TH}}{V_L} \right)$$

$$T = T_1 + T_2, \quad f = \frac{1}{T},$$


$$\text{Duty Cycle (Square)} \\ = \frac{T_1}{T_1 + T_2} * 100\%$$

$$\text{Duty Cycle (Triangular)} \\ = \frac{T_2}{T_1 + T_2} * 100\%$$

Special Case: When $V_L = -V_H$

$$T = T_1 + T_2 = \frac{4R_i C}{P}$$

$$f = \frac{1}{T} = \frac{P}{4R_i C}$$

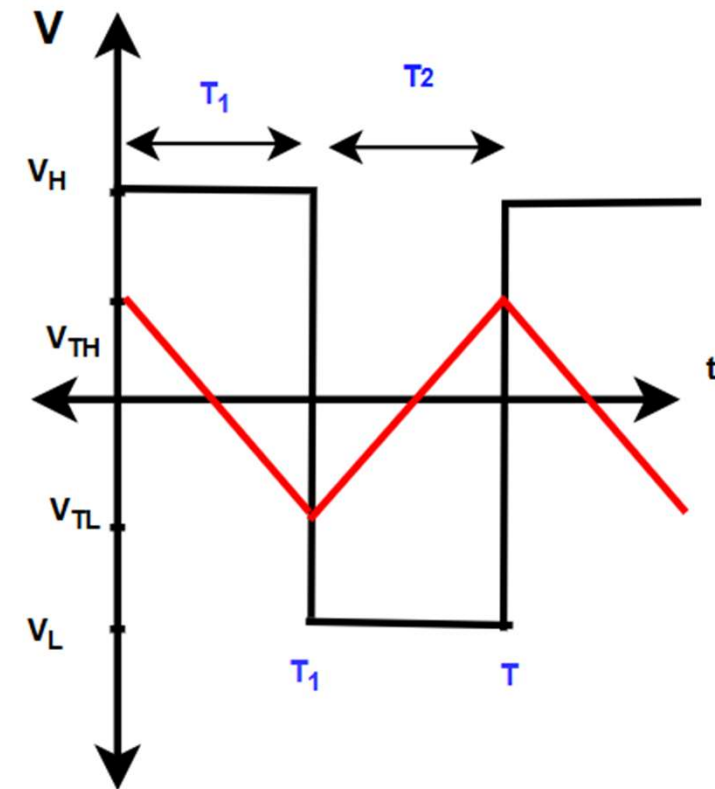


Exercise

Answer the following question for the Triangular wave generator.

Given, $R_i = 10k$, $C = 10 \mu F$, $R_2 = pR = 20k$,
 $R_1 = R = 10k$,

$V_L = -V_H$ or $V_H = 15 V$, $V_L = -15 V$

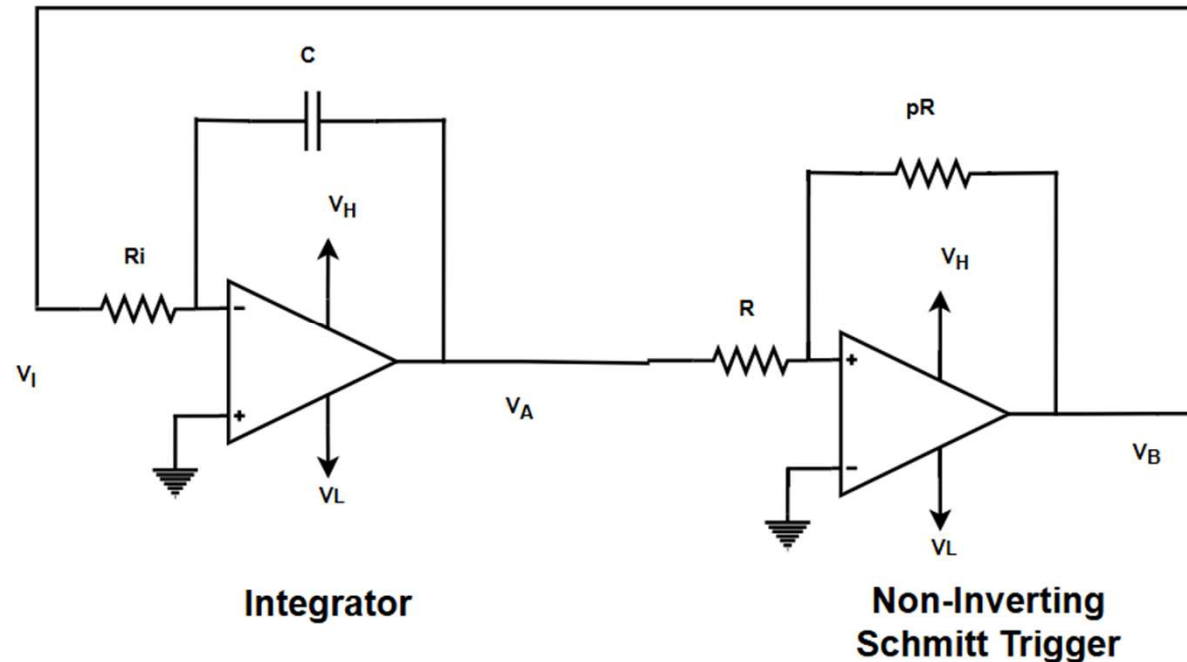- Draw the voltage V_A and V_B vs t plot with proper labeling.
- Draw the VTC of the Schmitt trigger.
- Find the frequency, Time period, Duty cycle of the Triangular wave, Duty cycle of the Square wave.



Exercise

Answer the following question for the Triangular wave generator.

Given, $R_i = 10k$, $C = 10 \mu F$, $R_2 = pR = 20k$,
 $R_1 = R = 10k$,

And, $V_H = 10 V$, $V_L = -12 V$

- Draw the voltage V_A and V_B vs t plot with proper labeling.
- Draw the VTC of the Schmitt trigger.
- Find the frequency, Time period, Duty cycle of the Triangular wave, Duty cycle of the Square wave.

