

CSE350: Digital Electronics & Pulse Techniques


Lecture 02: DAC

Course Instructor:



*MD. ZAYED BIN ZAHIR ARJU (ZBH), ADJUNCT LECTURER
Department of Computer Science and Engineering (CSE)
BRAC University*

Digital to Analog Converter (DAC)

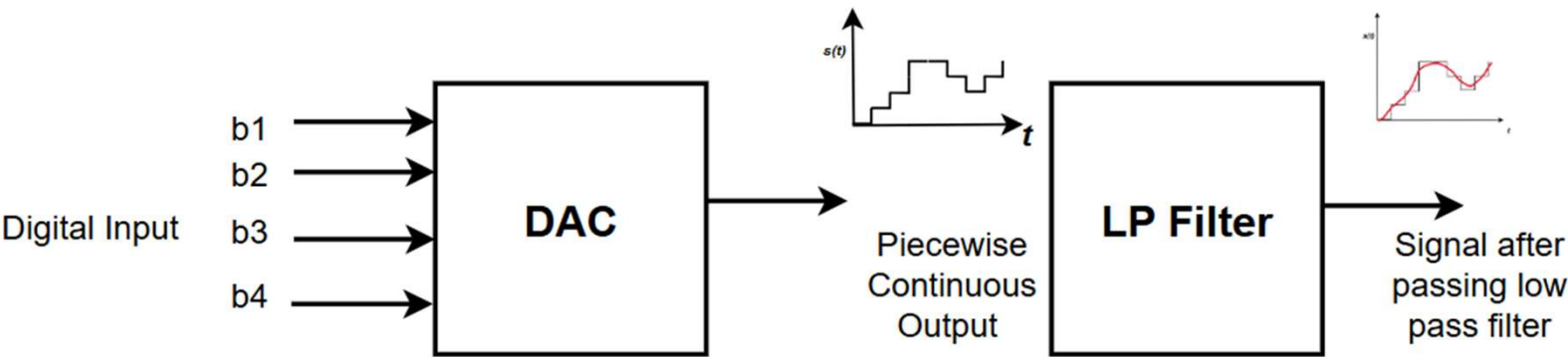

Binary to Decimal Conversion

Binary Number: $B_3B_2B_1B_0$

Equivalent Decimal Number: $B_3 * 8 + B_2 * 4 + B_1 * 2 + B_0 * 1$


Example : Convert 1001_2 value into a decimal value.

Solve: $1001_2 = 1 * 8 + 0 * 4 + 0 * 2 + 1 * 1 = 9_{10}$

Binary Weighted Resistor DAC

Key features of this circuit,

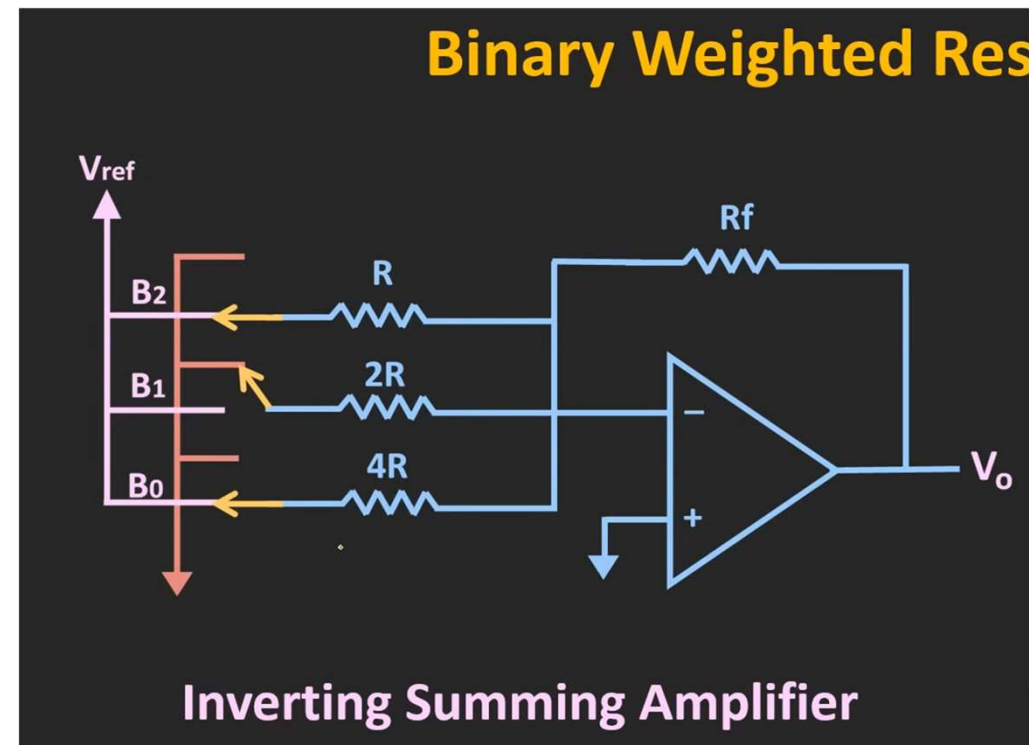- **LSB branch** will contain biggest resistor
- **MSB branch** will contain Smallest resistors
- Output will be positive if the **input voltage is negative**
- Resistor of adjacent branch will be either double or half
- There are **2^n output level** for **n bit input**.




Binary Weighted Resistor DAC

An inverting adder with a feedback resistor $R_f = R$ is used, along with doubling resistors at inverting input terminal. A switch is connected to all branches of input, which may connect to a reference voltage or ground. Since, no current flows through the input terminal of an op-amp and the non-inverting & inverting terminals are virtually shorted, the current towards & voltage at the inverting terminal are both 0.

Let, the current from output to the terminal through R_f is I . Then,
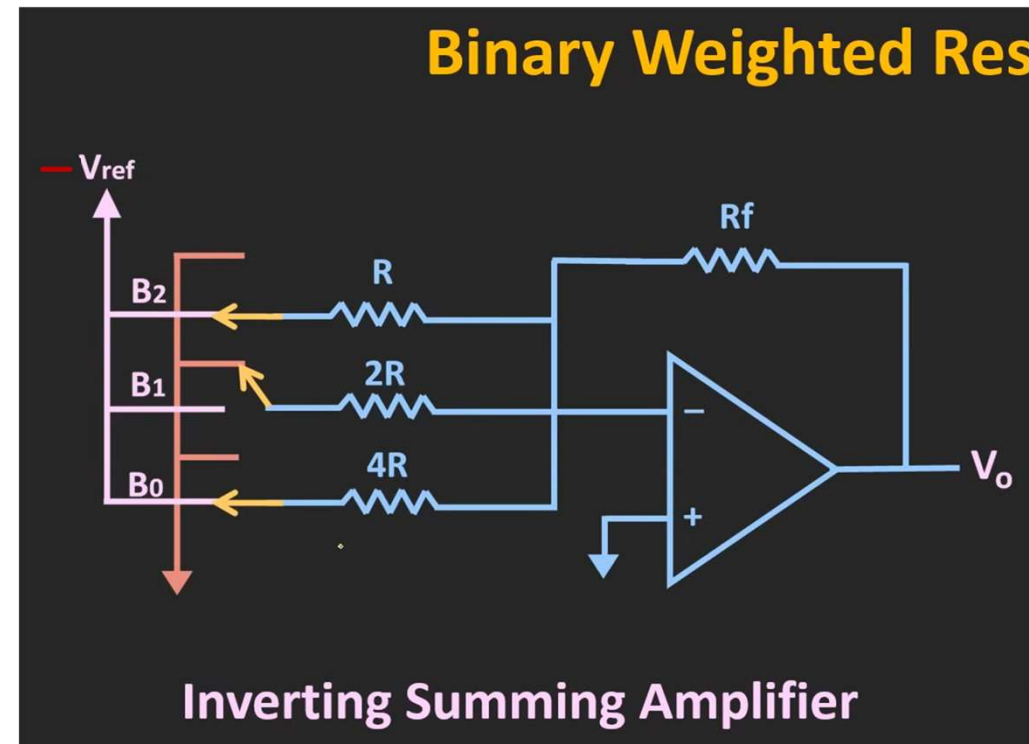
$$I = \frac{V_o - 0}{R_f} = I_2 + I_1 + I_0$$




Where, I_2 , I_1 & I_0 are the currents through the input branches. When the switches are connected to reference voltage, we can express these currents as,

$$I_2 = \frac{0 - (-V_{ref})}{R} \quad I_1 = \frac{0 - (-V_{ref})}{2R} \quad I_0 = \frac{0 - (-V_{ref})}{4R}$$

When the switches are connected to ground, the currents are 0. **The switches are actually implementations of the bits of the digital input signal.** These bits if assumed to be B2, B1, B0, then the currents can be expressed for both cases as,
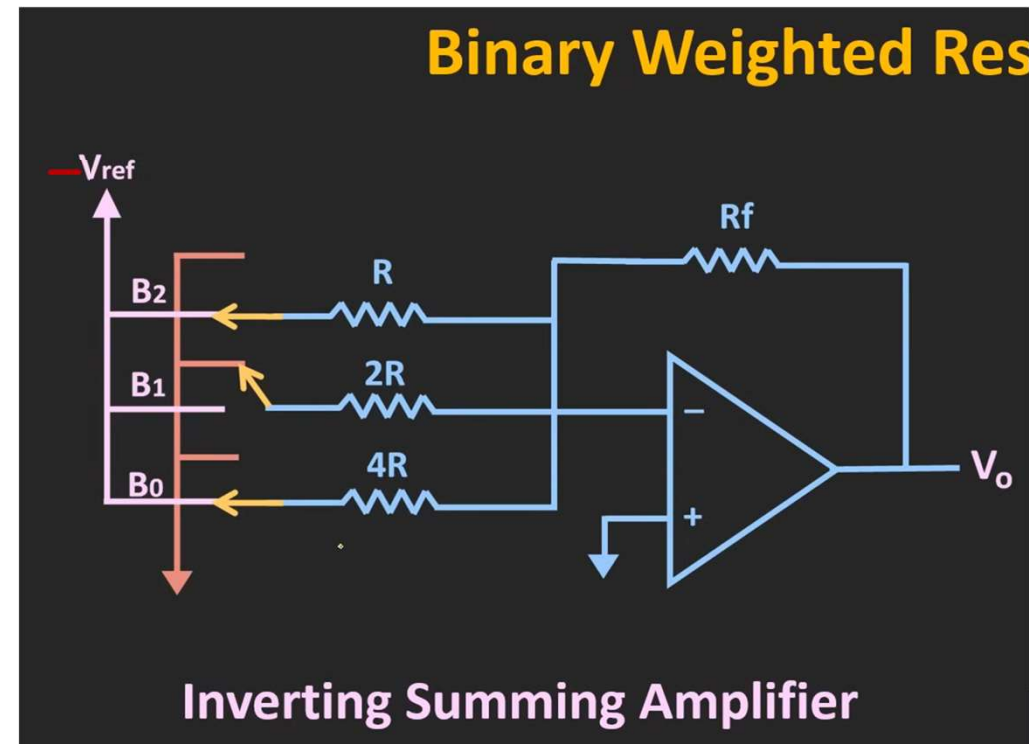
$$I_2 = B_2 \frac{V_{ref}}{R} \quad I_1 = B_1 \frac{V_{ref}}{2R} \quad I_0 = B_0 \frac{V_{ref}}{4R}$$



Applying KCL at inverting terminal,

$$I = \frac{V_o}{R} = I_2 + I_1 + I_0 = V_{ref} \left(\frac{B_2}{R} + \frac{B_1}{2R} + \frac{B_0}{4R} \right)$$

$$V_o = V_{ref} \left(B_2 + \frac{B_1}{2} + \frac{B_0}{4} \right)$$

The highest output voltage is,

$$V_o = V_{ref} \left(1 + \frac{1}{2} + \frac{1}{4} \right) = V_{ref} \frac{8 - 1}{4} = V_{ref} \frac{2^n - 1}{2^{n-1}}$$

One of the **disadvantages** of Binary Weighted Resistors is that, **a lot of resistors are used**. Hence, **fluctuations in their values** can cause errors in output voltage. This sensitive nature can be overcome by **the R-2R Ladder DAC**.


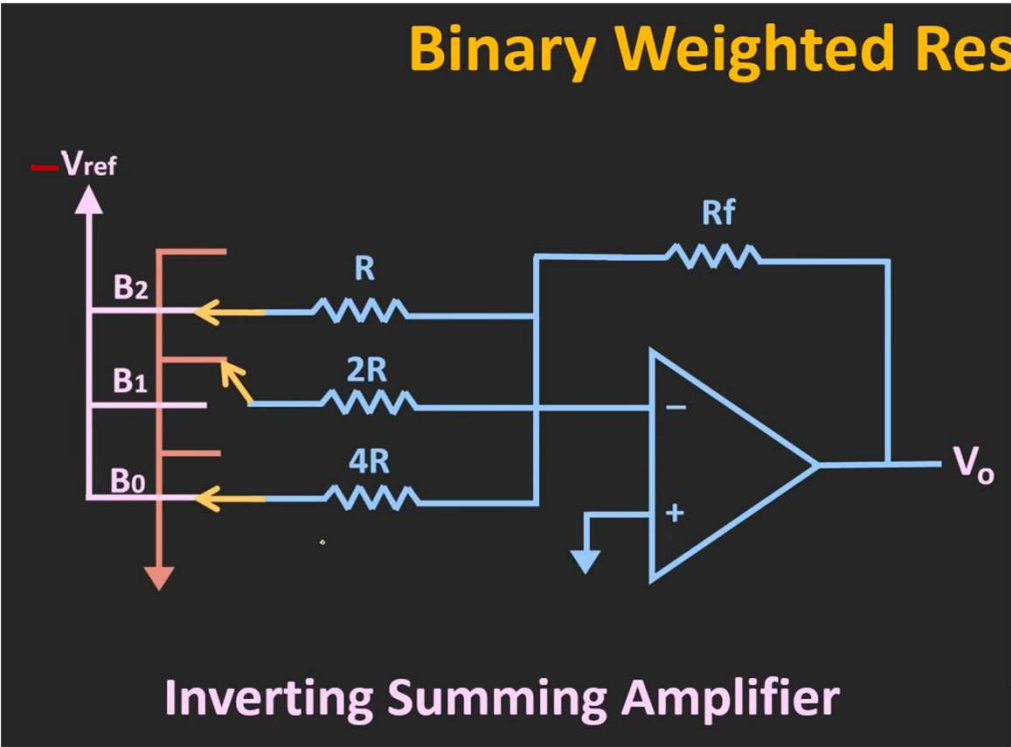


Table: For different input combination. Combination = $2^3 = 8$,

B0	B1	B2	Vo
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Suppose,
 $V_{REF} = 8\text{ V}$

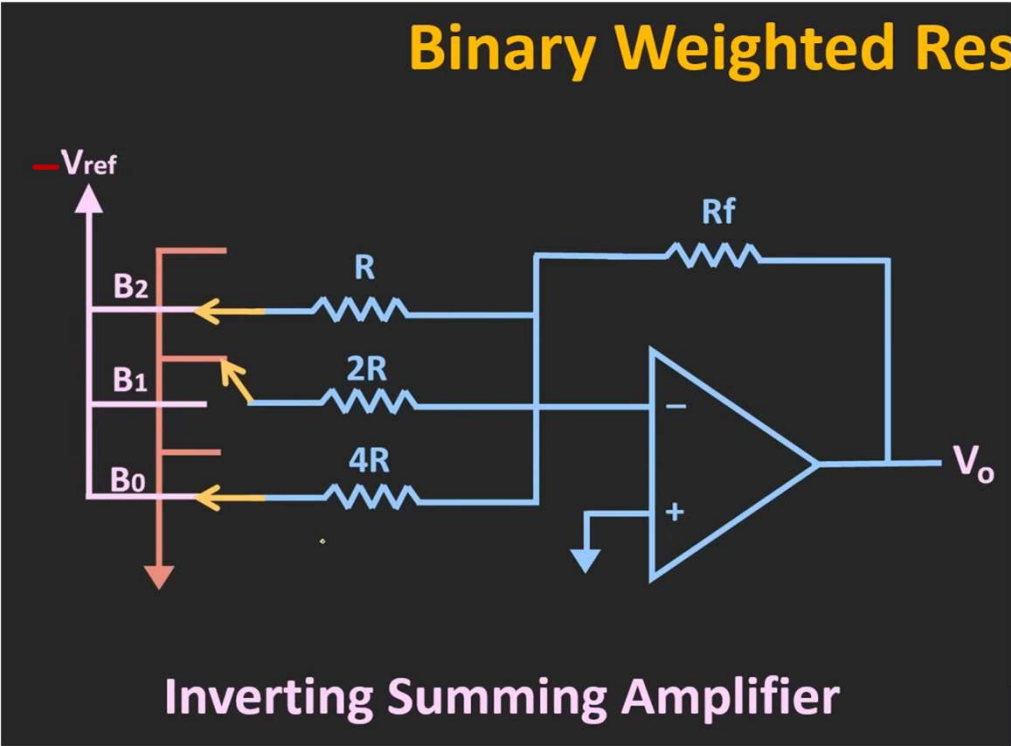


- If $V_{REF} = 8\text{ V}$, what will be the step size ?

Step size is the difference between two adjacent output values or the output value for the LSB bits contribution only. For **0001 input**, output will be the step size.

- If $V_{REF} = 8\text{ V}$, what will be the Max output ?

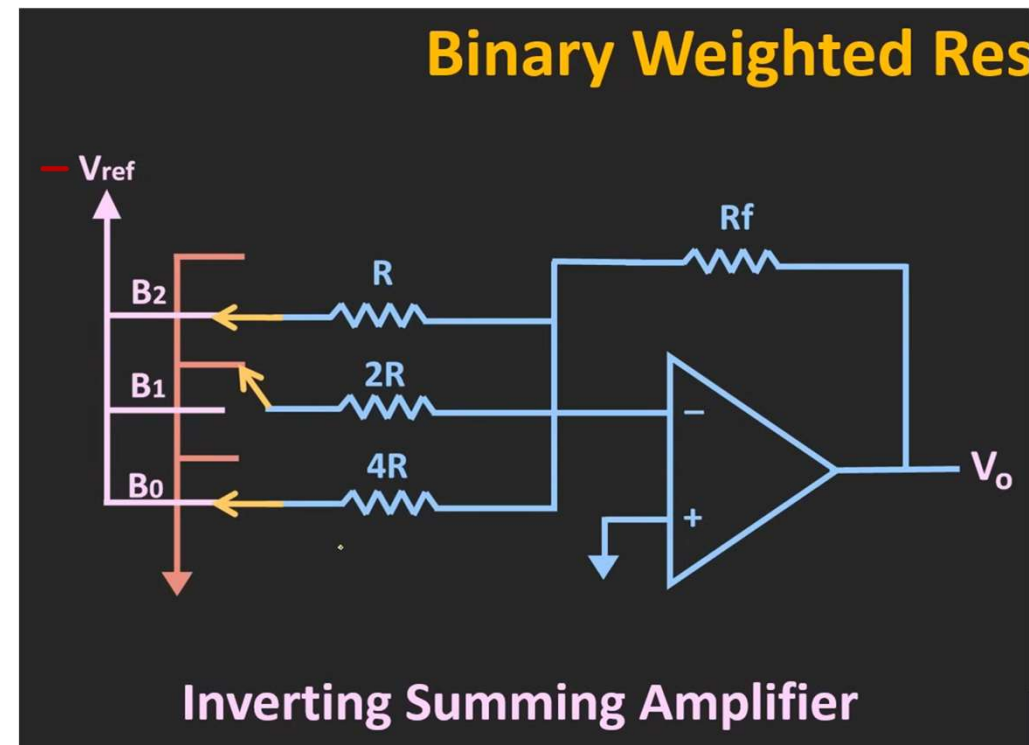Max output level can be found for high input at every input. For **1111 input**, output will be max.



General Format for DAC

Binary: DCBA

$$V_o = -R_f \left(\frac{V_D}{R_D} + \frac{V_C}{R_C} + \frac{V_B}{R_B} + \frac{V_A}{R_A} \right)$$

$R_A > R_B > R_C > R_D$ and factor of 2

If we assign,

$R_D = R$, then, $R_C = 2R$, $R_B = 4R$, $R_A = 8R$


If we assign,

$R_A = R$, then, $R_B = R/2$, $R_C = R/4$, $R_D = R/8$

If we want, positive output, V_{REF} need to be negative.

If we want, negative output, V_{REF} need to be positive.

DESIGN 4-bit DAC

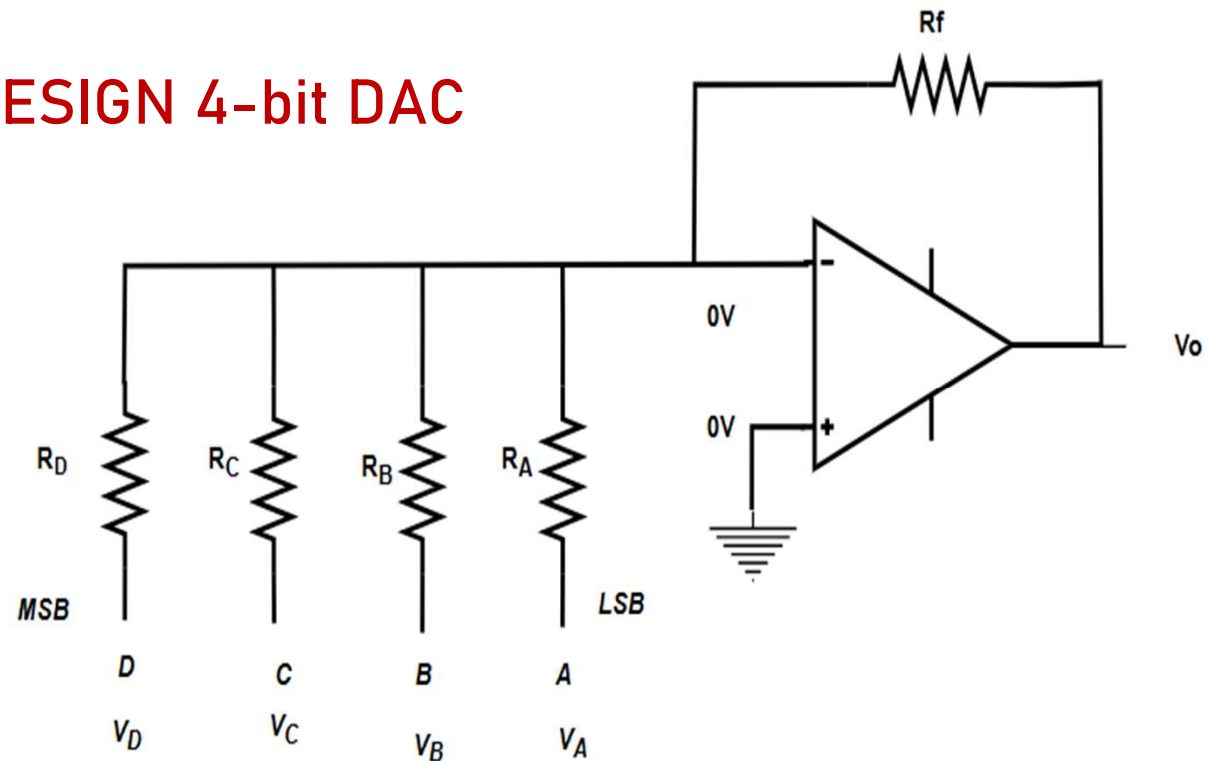

DAC (MSB → R)

Binary: DCBA


If $V_A = A * V_{REF}$, $V_B = B * V_{REF}$,
 $V_C = C * V_{REF}$, $V_D = D * V_{REF}$

$R_D = R$, then, $R_C = 2R$, $R_B = 4R$, $R_A = 8R$

$$V_o = -\frac{R_f}{R} \left(V_D + \frac{V_C}{2} + \frac{V_B}{4} + \frac{V_A}{8} \right)$$

$$V_o = -\frac{R_f * V_{REF}}{R} \left(D + \frac{C}{2} + \frac{B}{4} + \frac{A}{8} \right)$$

DESIGN 4-bit DAC

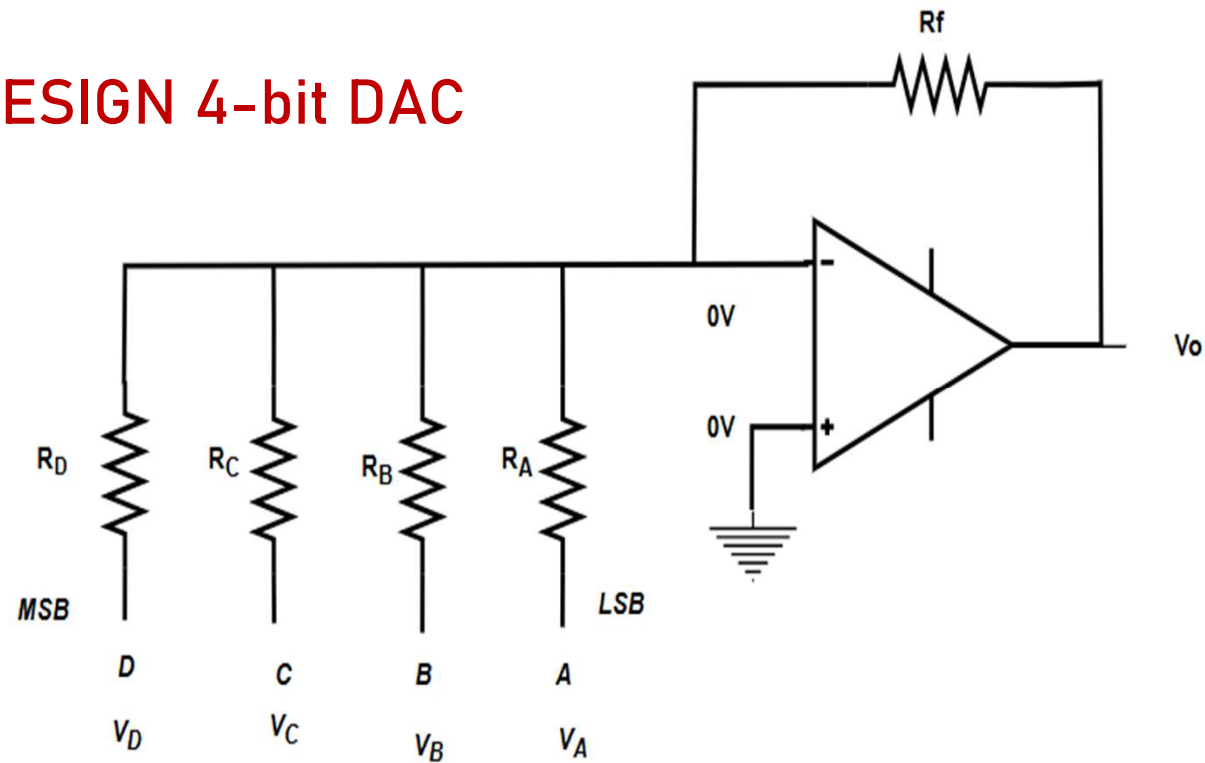

DAC (LSB \rightarrow R)

Binary: DCBA


If $V_A = A * V_{REF}$, $V_B = B * V_{REF}$,
 $V_C = C * V_{REF}$, $V_D = D * V_{REF}$

$$R_A = R, R_B = \frac{R}{2}, R_C = \frac{R}{4}, R_D = \frac{R}{8}$$

$$V_o = -\frac{R_f}{R} (8 * V_D + 4 * V_C + 2 * V_B + 1 * V_A)$$

$$V_o = -\frac{R_f * V_{REF}}{R} (8 * D + 4 * C + 2 * B + 1 * A)$$

DESIGN 4-bit DAC

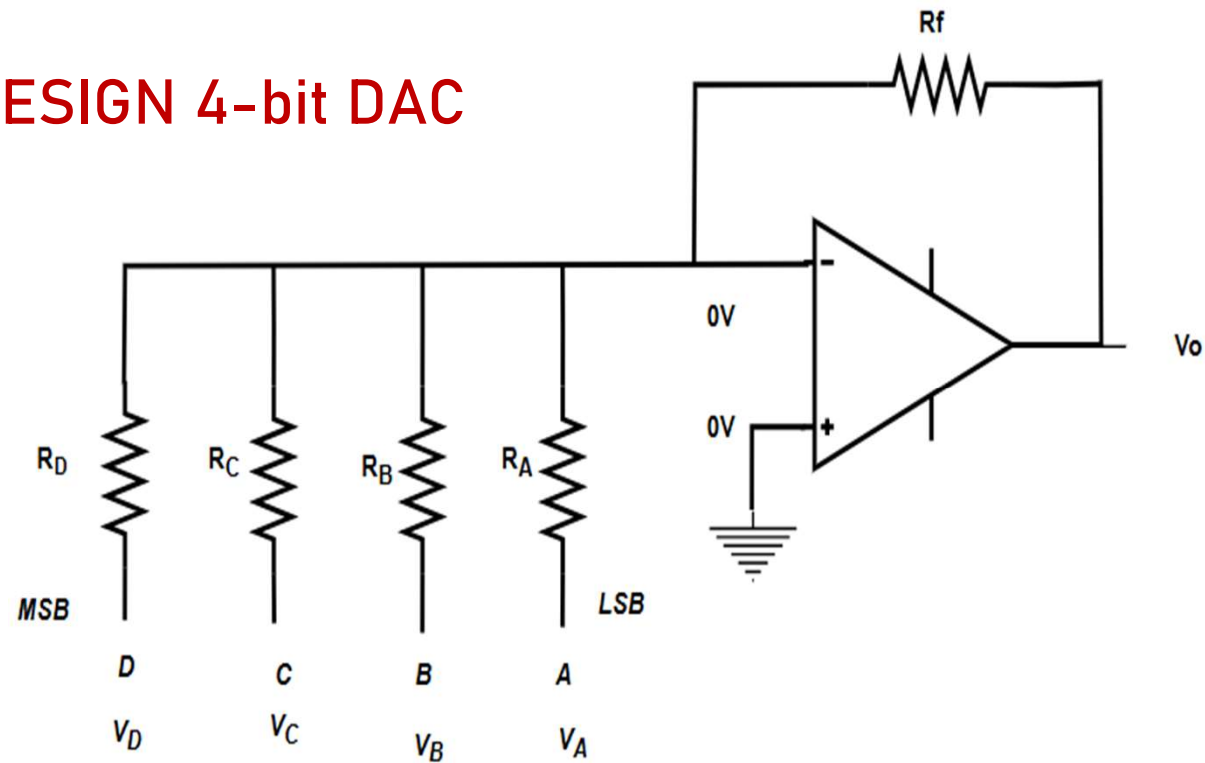


Exercise -


Binary: DCBA

If $R_A = R_F = 10k\Omega$, Find the following parameter for this DAC circuit. Given, $V_{REF} = 0.5\text{ V}$, $V_H = 30\text{ V}$ and $V_L = -30\text{ V}$

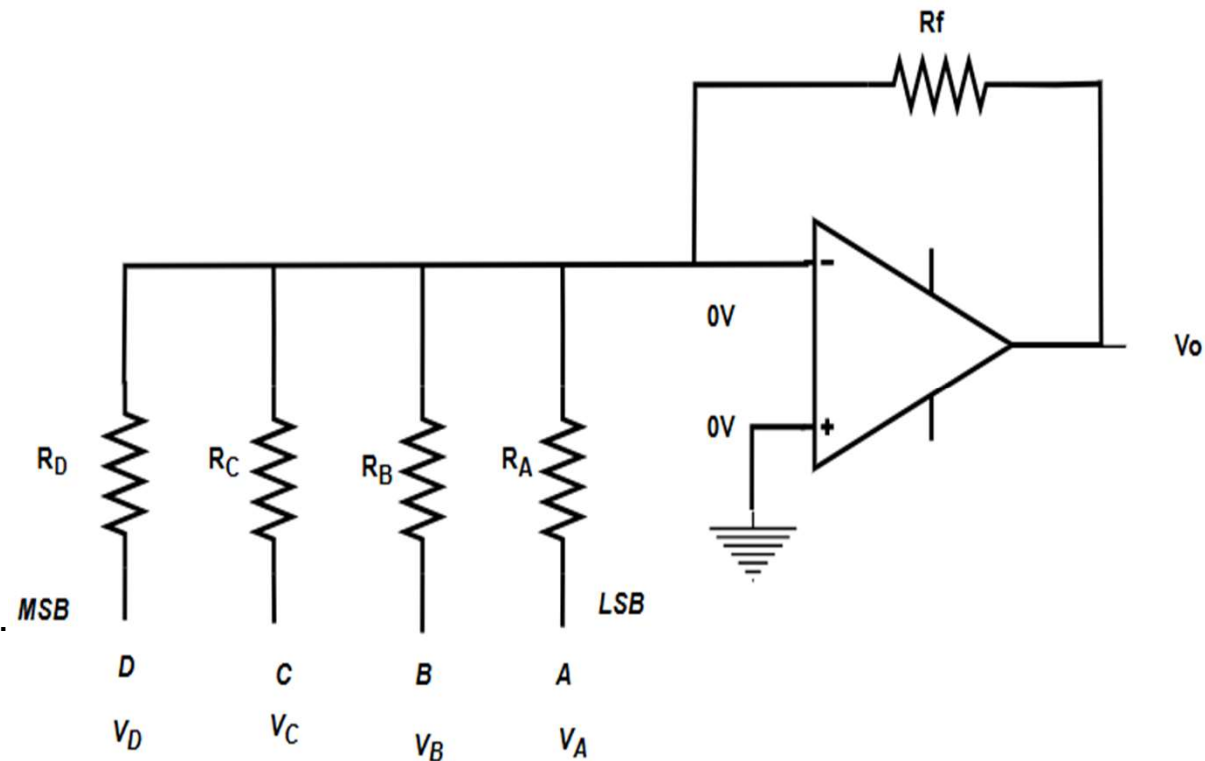- Find the value of maximum output.
- Find the value of the step size.
- Find the value of the 1-LSB change voltage.
- Find the value of the 1-MSB change voltage.
- Plot the Output voltage vs input binary.




R2R Ladder DAC: beside is shown a **3-bit R2R ladder DAC**. Here, as we can see, a resistive network of **R & 2R** is used, which has a ladder type structure. The switches connected in 2R branches can either connect to the ground at inverting terminal or that at the non-inverting terminal. In the former case, the current can flow through the feedback resistor 2R. But when the switch connects to non-inverting terminal, it flows to ground.

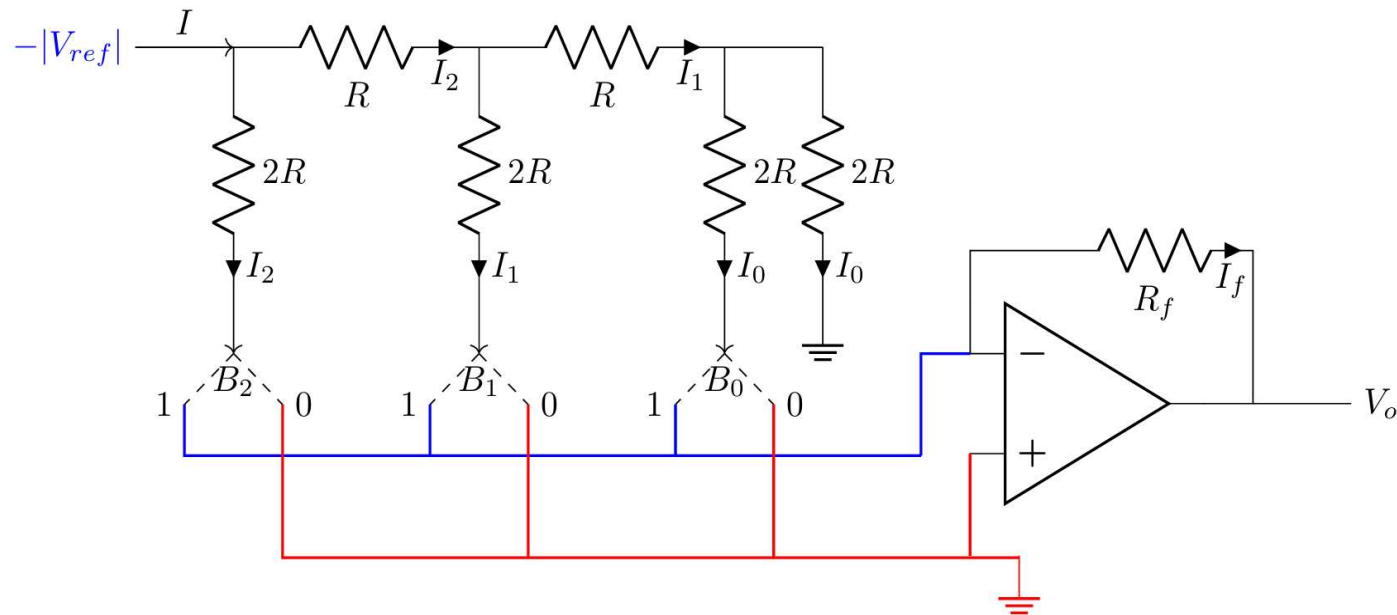

$$I = 2I_2 = 2 * 2I_1 = 2 * 2 * I_0 = 8I_0$$

Also,
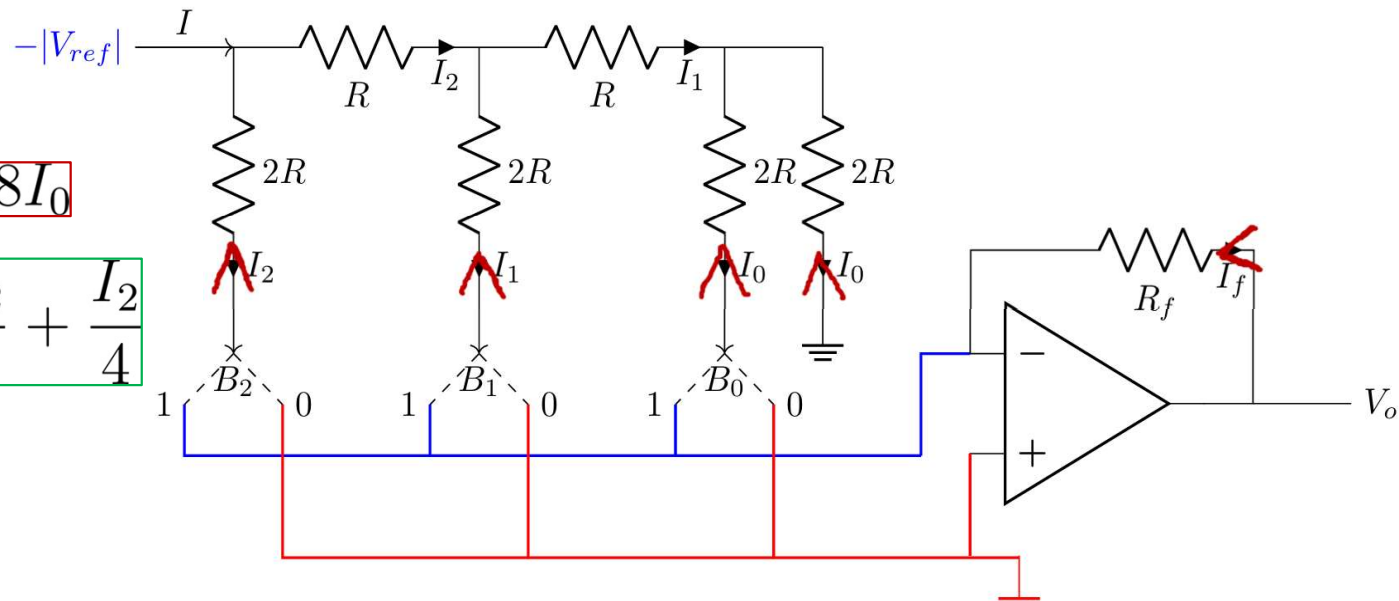
$$I_2 = \frac{0 - (-V_{ref})}{2R} = \frac{V_{ref}}{2R}$$




Thus, the current through the feedback resistor $2R$ can be expressed using KCL at inverting terminal,

$$I = B_2 \frac{V_{ref}}{2R} + B_1 \frac{V_{ref}}{4R} + B_0 \frac{V_{ref}}{8R} = \frac{V_o - 0}{2R}$$

So,
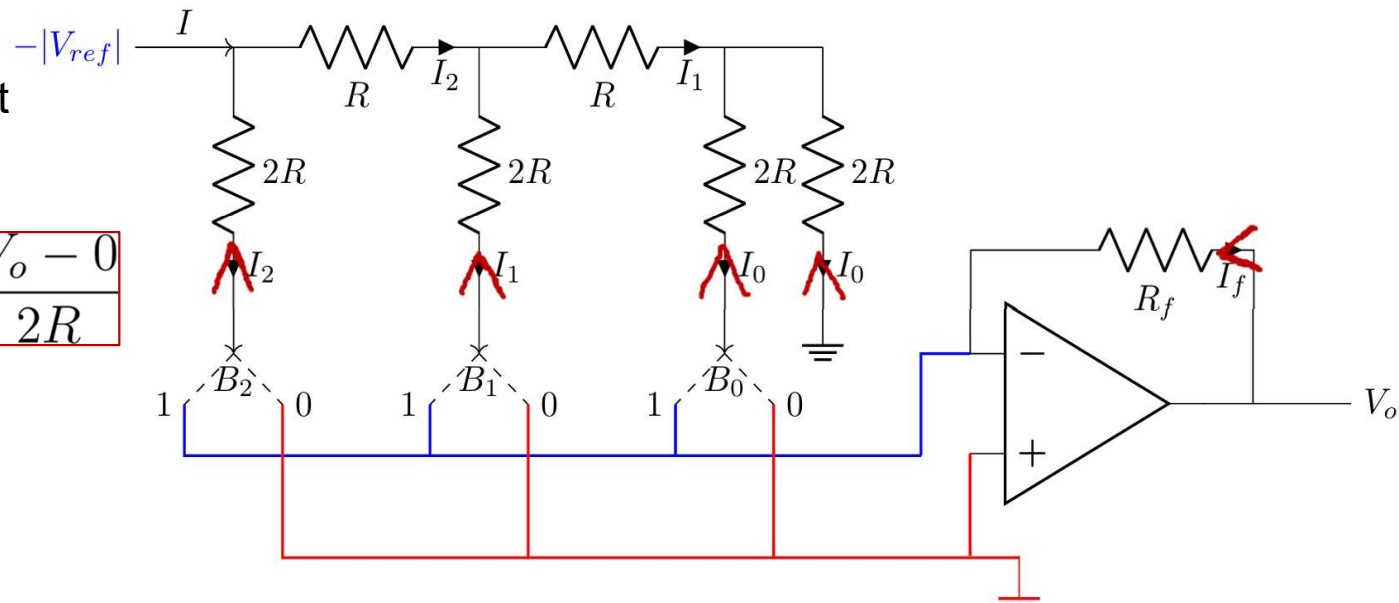
$$V_o = V_{ref} \left(B_2 + \frac{B_1}{2} + \frac{B_0}{4} \right)$$



Exercise -

The figure below shows the input-output characteristics of a converter. The output of the converter is denoted as V_o and the input as V_{in} . Identify the converter type and the number of bits used by the converter. Further, calculate V_{ref} when $RF = 2R$.

