

# Assignment 01

Course: CSE 350

Summer 2025

(Total Marks - 30)


## Question – 01

CO3

10 marks

$R = 10\text{k}\Omega$ ,  $V_{\text{fullrange}} = 10\text{ V}$  (Reference Voltage).

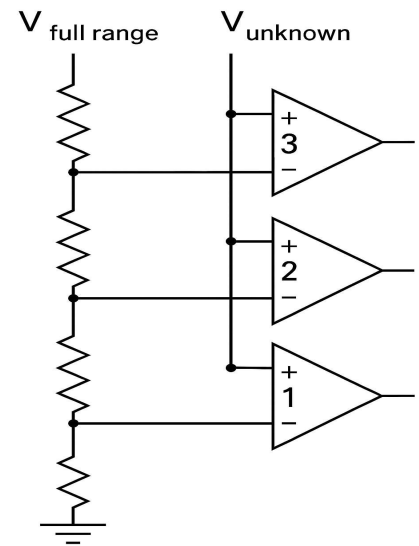- What will be the output binary bits line for the above circuit?
- Draw the quantization level vs Input signal plot.
- If  $V_{\text{unknown}} = 3.5\text{ V}$ , what will be the quantization error for this case? (Hint: Quantization error = Actual value - Quantized value)



## Question – 02

CO3

10 marks

$$x(t) = 5 + 5 \sin(2\pi ft) \text{ V}$$

Where  $f = 2\text{ kHz}$ .


The above signal will be converted to a digital signal through an ADC circuit.

- What will be the minimum required sampling frequency for this signal?
- Suppose the sampling frequency is set at  $10\text{ kHz}$ . Find the first 5 sampling values as well as their corresponding quantized value and encoded value.

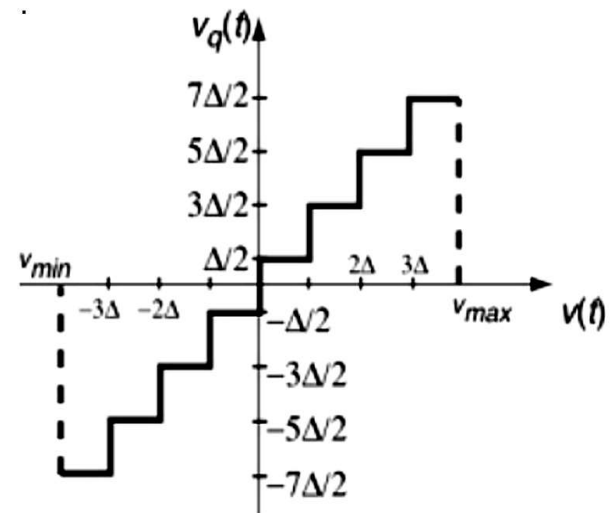**Question – 03****CO3****10 marks**

The following plot is the relationship between input and output of a midrise quantizer. Where the step size is  $2V$ .

- What is the number of binary bits required to express the quantization levels?
- Find the corresponding quantized value if the inputs of the quantizer are  $-5.6\text{ V}$  and  $7.34\text{ V}$ .
- What will be the maximum value of the quantization error?
- Design a full ADC circuit consisting of maximum current of the circuit should not exceed  $0.1\text{ mA}$ .



midrise quantizer